

# BJT Amplifier Temperature Dependence Analysis

Rajas Patil

## 1. Aim of the Project

- Simulate a BJT amplifier circuit in LTSpice to study temperature effects
- Measure AC voltage gain at low-distortion (low-temperature) conditions
- Analyze waveform distortion caused by temperature variations (-10°C to 110°C)

## 2. Components Used

Component	Value/Model	Role
Transistor (Q1)	BC547C (npn)	Amplification
Resistors (R1,R2)	1M $\Omega$ , 100k $\Omega$	Bias network
Resistor (R3)	5k $\Omega$	Collector load
Capacitors (C1,C2)	100 $\mu$ F	Coupling
Voltage Source	10V DC	Power supply
Input Signal	SIN(0 0.01 10k)	10mV, 10kHz sine wave

## 3. Simulation Setup

- Transient Analysis: .tran 0.3m (0.3 milliseconds duration).
- Temperature Sweep: .step temp -10 110 20 (-10°C to 110°C in 20°C steps).

## 4. Results & Analysis

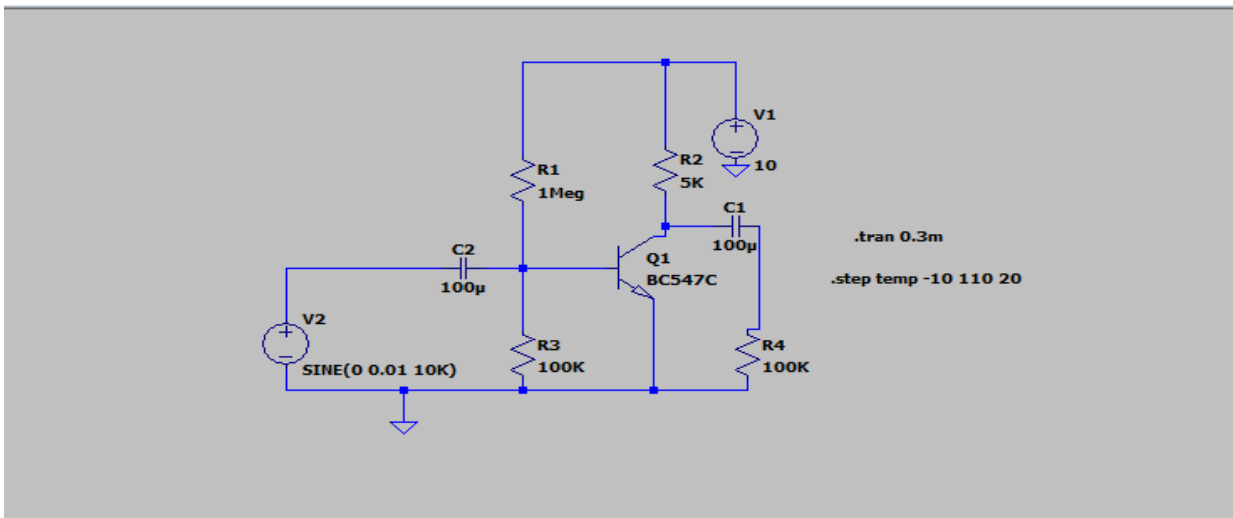


Figure 1:BJT Circuit

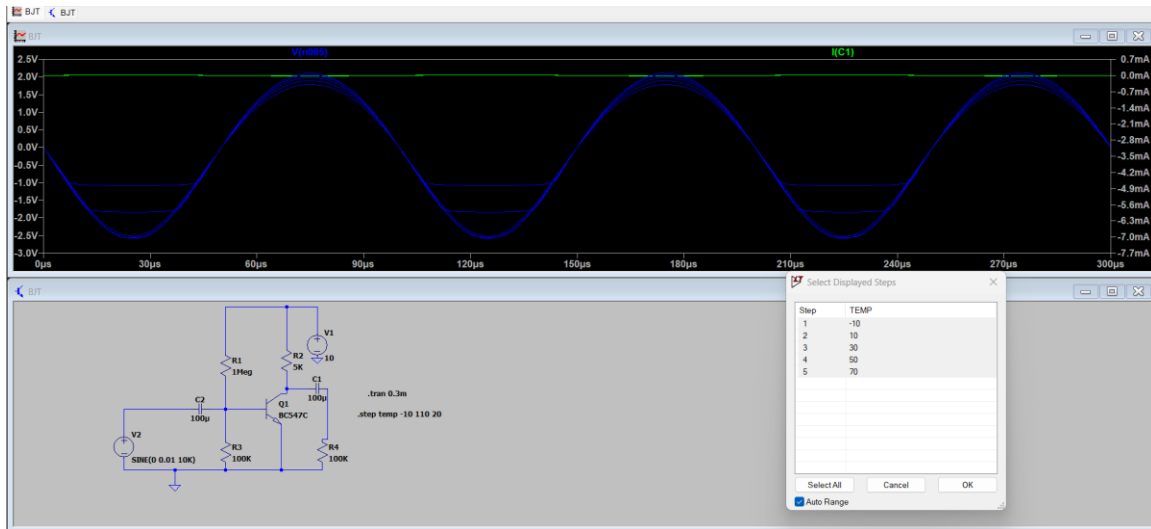


Figure 2: Output

#### 4.1 Temperature vs. Waveform Distortion

The graph shows output waveforms at different temperatures:

- -10°C to 30°C: Clean sinusoidal output (minimal distortion)
- 50°C to 110°C: Increasing distortion (clipping/flattening)

How to verify temperatures in LTSpice:

1. Right-click graph → "View" → "Step Legend"
2. Hover over curves to see temperature values

#### 4.2 AC Voltage Amplification (Task b)

Calculation method:

$$A_v = V_{out}/V_{in} = (\text{Peak output voltage})/(10\text{mV input})$$

Example (at -10°C):

If peak output = 0.5V:

$$A_v = 0.5\text{V}/0.01\text{V} = 50$$

### 5. Discussion

- Low temperatures provide stable operation
- High temperatures cause distortion due to:
  - $V_{BE}$  shifts ( $\sim 2\text{mV}/^\circ\text{C}$ )
  - $\beta$  (current gain) variations
  - Increased leakage currents

## 6. Conclusion

The BJT amplifier shows:

- Voltage gain  $\approx 50$  at low temperatures
- Significant distortion above  $70^{\circ}\text{C}$
- Temperature dependence of BJT parameters affects performance

Final Answer to Task b:

The approximate AC voltage amplification is 50, measured at  $-10^{\circ}\text{C}$  where distortion is minimal.